



## MEC4126F: Integrated Embedded Systems

Prac 7  
08 May 2025

Total marks: 51

---

### Instructions to students

1. This template file contains space for the answers to the written questions of Prac 7.
2. Ensure that you copy-paste your answers inside the space allocated for each question.
3. Provide your numerical answers to **TWO (2)** significant decimal points, unless stated otherwise.


<b>PeopleSoft ID: 1879813</b>
-------------------------------

## Plagiarism Declaration

By demonstrating and submitting this practical I agree that:


- I know that plagiarism is a serious form of academic dishonesty.
- I have read the document about avoiding plagiarism, am familiar with its contents and have avoided all forms of plagiarism mentioned there.
- Where I have used the words of others, I have indicated this by the use of quotation marks.
- I have referenced all quotations and other ideas borrowed from others.
- I have not and shall not allow others to plagiarise my work.
- I have not used an AI language model to generate the code or answers submitted here.

Name: **Daniele Sguazzin**

Signature: 

---

**Question 1 (6 marks)**

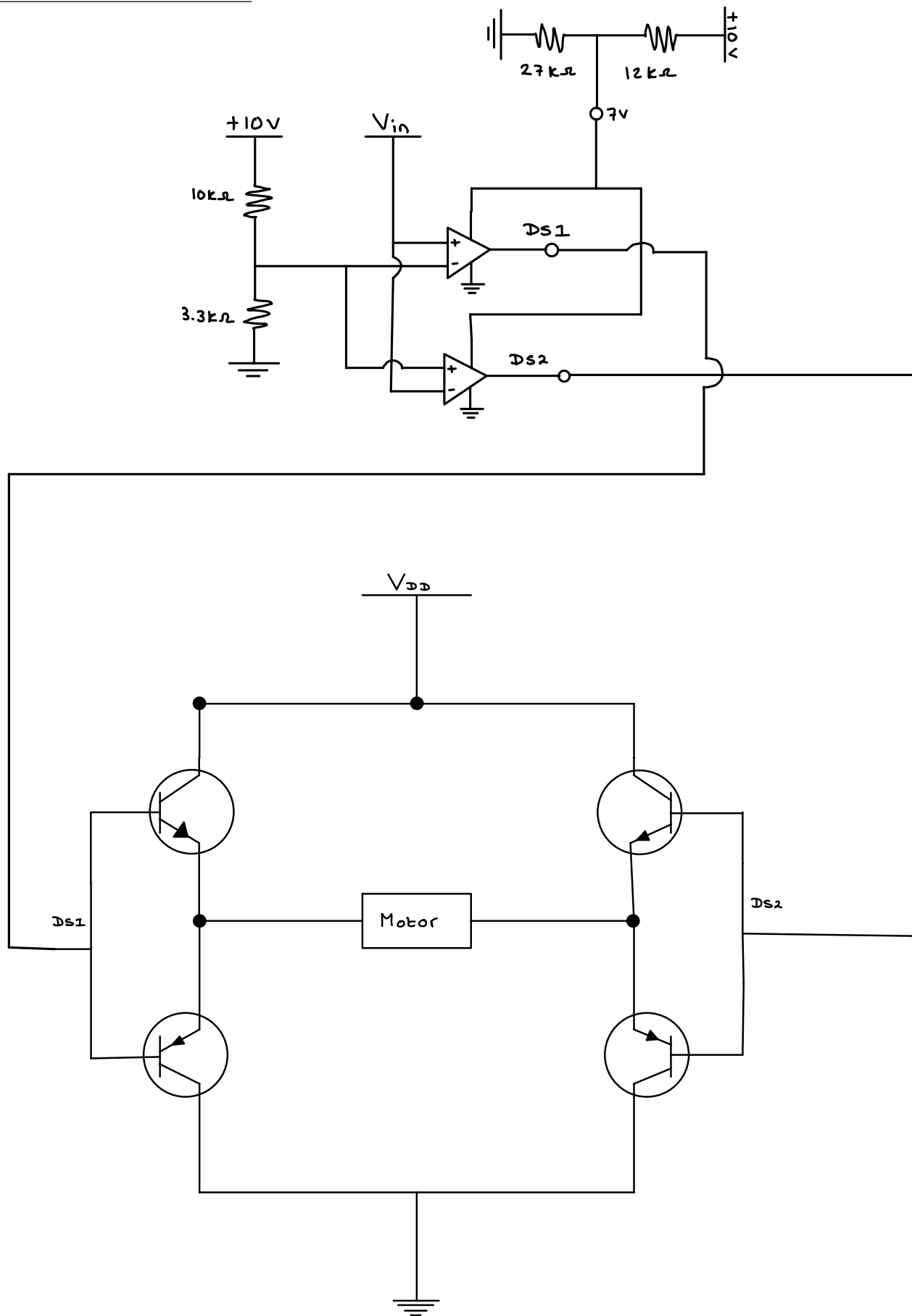

Question 2 (3 marks)


$V_{in}$	Comparator Output A (V)	Comparator Output B (V)
$> V_{ref}$	8.4	0.7
$< V_{ref}$	0.6	8.5

---

Question 3 (3 marks)

Comparator Output A (V)	Comparator Output B (V)	H-bridge direction
$\approx 8.5$	$\approx 0.6$	Forward
$\approx 0.5$	$\approx 8.4$	Reverse

Question 4 (14 marks)

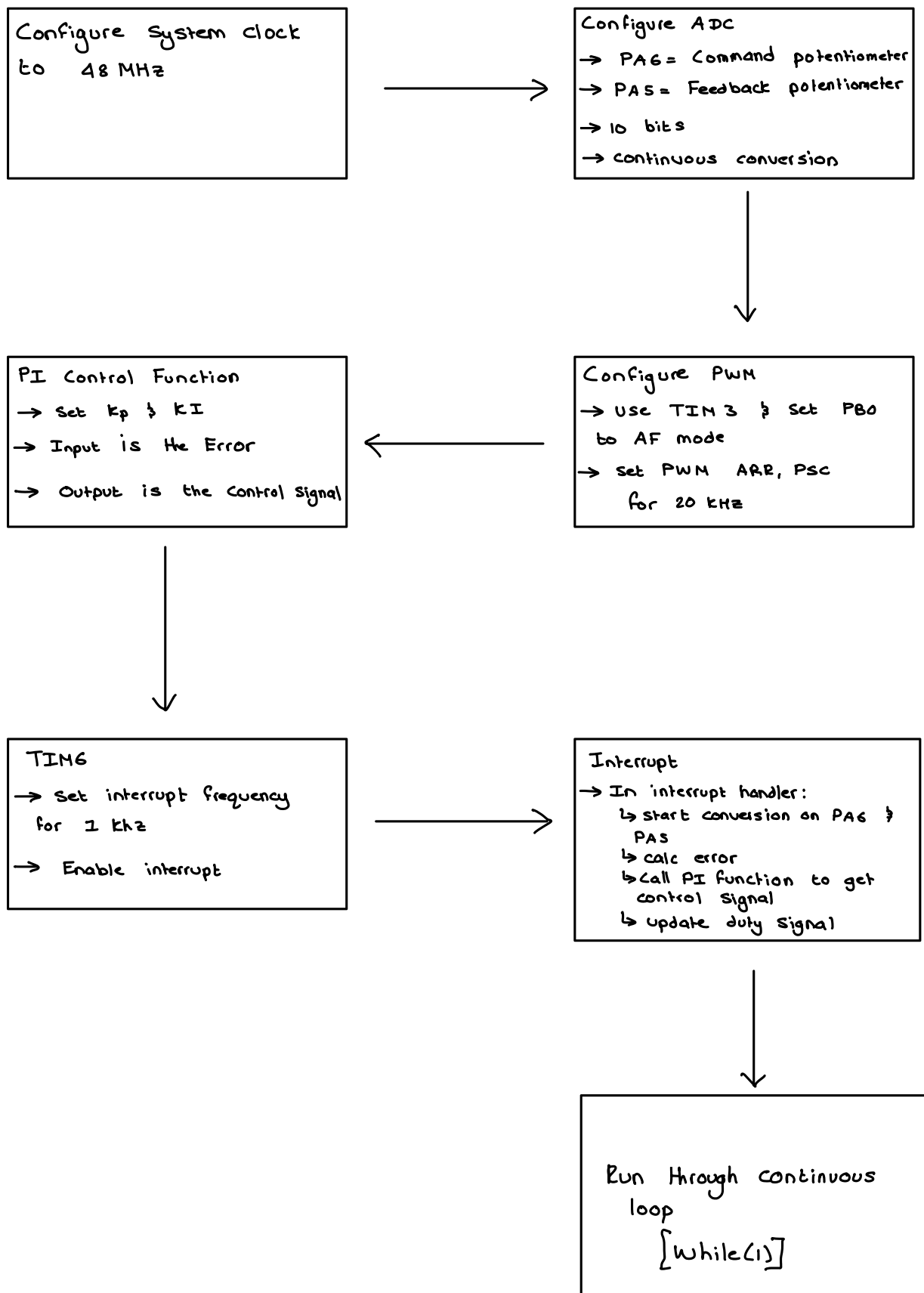

### Question 5 (6 marks)

Proportional gain

↳ Increase system response speed

↳ Too high: overshoot

Integral gain

↳ Eliminates steady-state error

↳ Too high: slow response

Sample Time

↳ Determines control loop frequency

↳ Too long: poor control

↳ Too short: unnecessary processor load

---

### Question 6 (10 marks)

(a) Slew rate  $\approx 0.5 \text{ V}/\mu\text{s}$

$$7\text{V} \Rightarrow t = \frac{7}{0.5} = 14 \text{ } \mu\text{s}$$

$$T_{\text{PWM}} > \frac{14 \text{ } \mu\text{s}}{0.01} = 1.4 \text{ ms}$$

$$f_{\text{PWM}} < \frac{1}{1.4 \times 10^{-3}} \approx 714.286 \text{ Hz}$$

$$\therefore \text{max freq} = 714 \text{ Hz}$$

$$T = \frac{(PSC+1)(ARR+1)}{48 \times 10^6}$$

$$\text{Let } PSC = 60$$

$$\therefore 1.4 \times 10^{-3} = \frac{(60+1)(ARR+1)}{48 \times 10^6}$$

$$\therefore ARR = 1100$$



